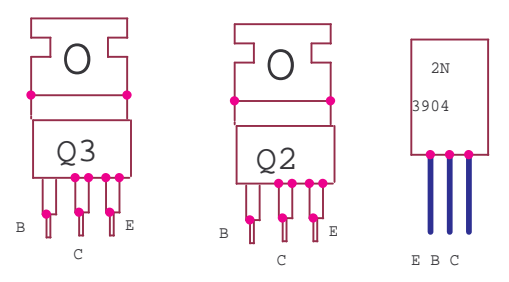


D2 IS A FREEWHEELING DIODE
 INDUCTIVE KICKBACKS ARE SHORTED BY THIS
 USE A FAST REC. DIODE FOR BETTER PERFORMANCE.

DC SOLID STATE RELAY

CONTROL - DC, 3-30V

OUTPUT - DC, 25V, 5A



CIRCUITS PROVIDED BY ANANTHA NARAYAN DELABS ARE FOR EDUCATIONAL PURPOSE ONLY.
 THE CIRCUITS ARE NOT PROVEN WORKING DESIGNS BUT CAN BE EXPERIMENTED UPON.
 THE USER OF THIS CIRCUIT WILL EXPERIMENT/APPLY/BUILD PROJECTS AT HIS OWN RISK.

Anantha Narayan delabs		
#2590, 17th Cross, 8th Main Banashankari 2nd Stage BANGALORE 560 070 Kar. India anantha_narayan@hotmail.com +91 80 6768863		
Title DC Control DC Load SSR		
Size B	Document Number DACT0012.SCH	Rev 00
Date: Sunday, August 10, 2003	Sheet 1	of 1